



Inspiring Excellence

Electronic Devices & Circuits (CSE251)

Submission by: **Tahmid Iqbal**

Student ID: **21201701**


Section: 06

Submission Date: 30.10.23

Group no: 04

ClassWork

Task01

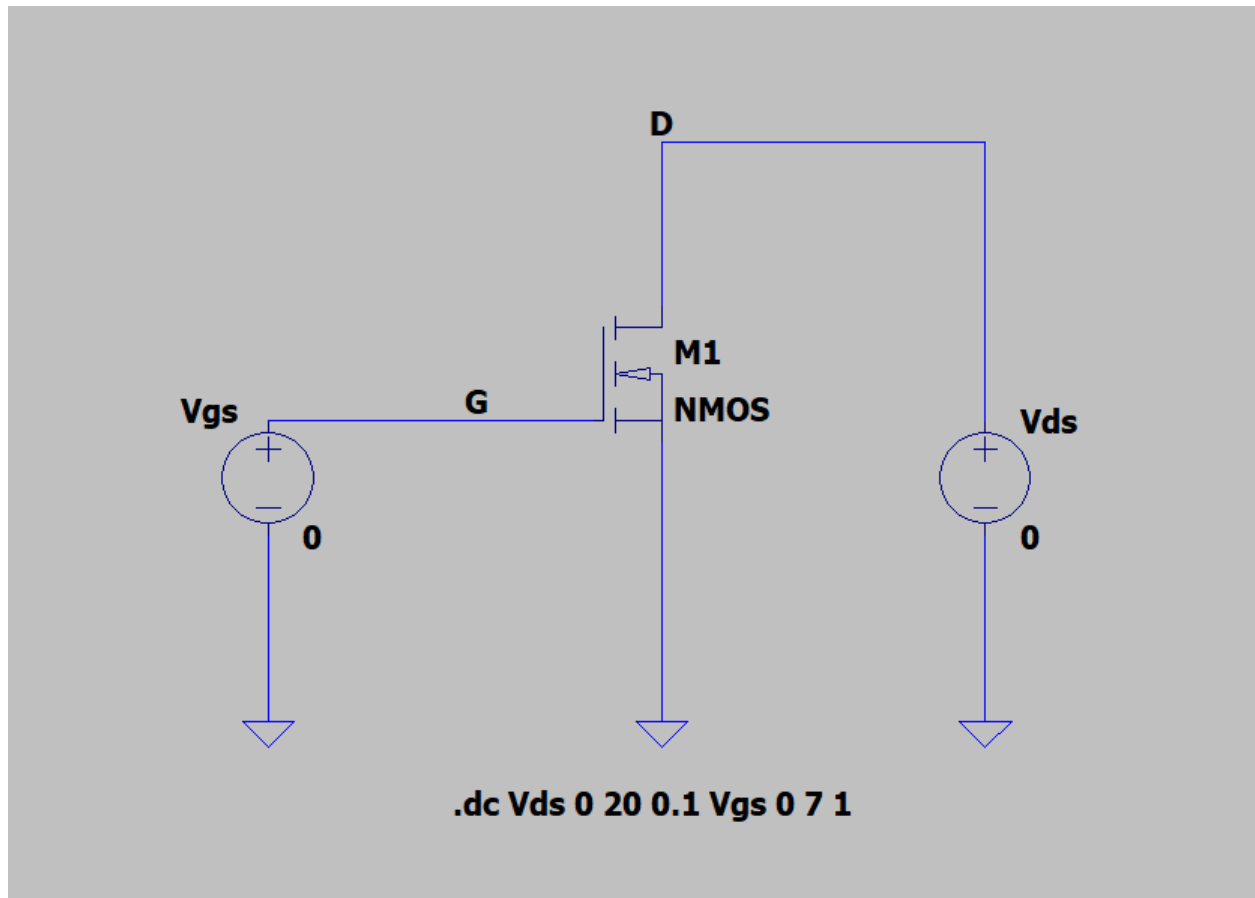


Data Table 1: Verification of the Truth Tables of Logic Gate and Logic Function

1. NAND Gate

Input Voltage, <u>V_x</u> (volt)	Input Voltage, <u>V_y</u> (volt)	V(output) (volt)	Boolean Output (0 or 1)
0V	0V	5	1
0V	5V	5	1
5V	0V	5	1
5V	5V	0.90098	0



Task01Part02

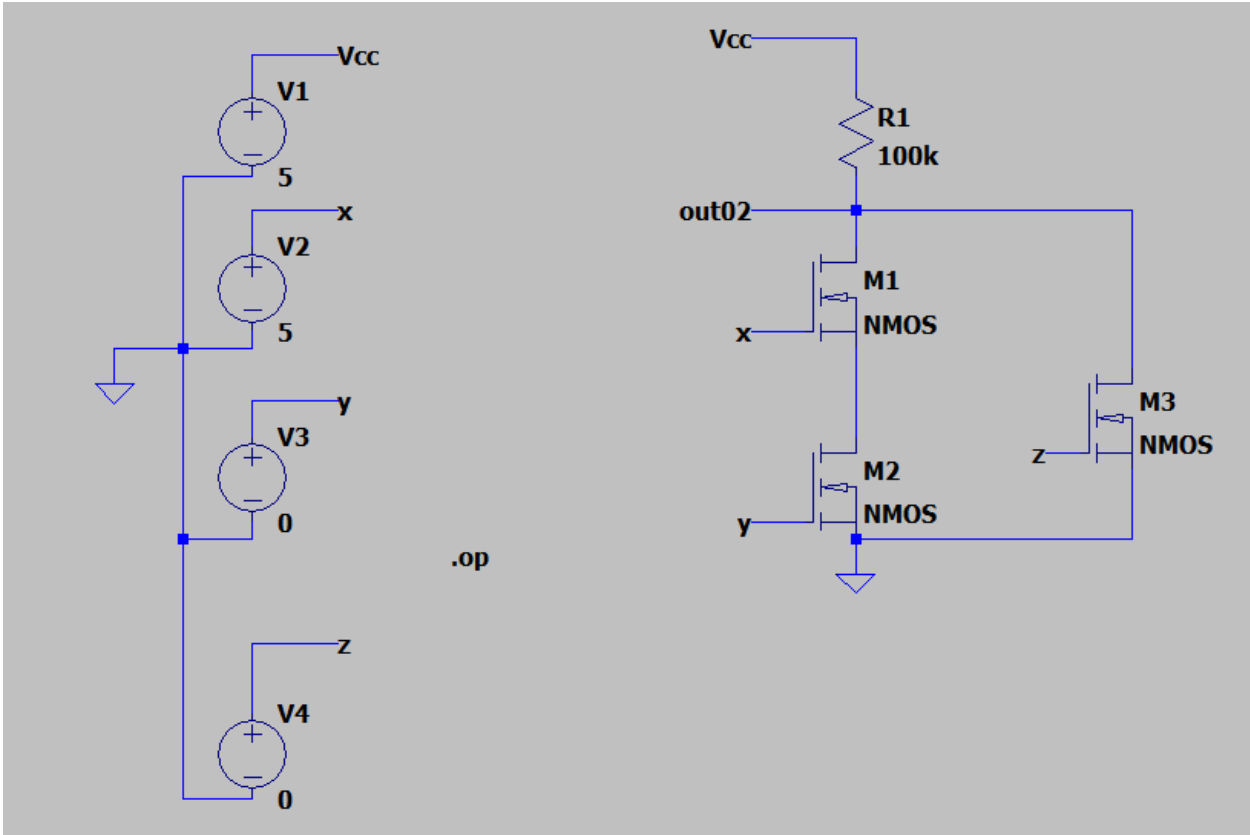

2. Logic Function, $f = \overline{xy} + \overline{z}$

Input Voltage, V_x (volt)	Input Voltage, V_y (volt)	Input Voltage, V_z (volt)	V(output) (volt)	Boolean Output (0 or 1)
0V	0V	0V	5	1
0V	0V	5V	0.475062	0
0V	5V	0V	5	1
0V	5V	5V	0.475062	0
5V	0V	0V	5	1
5V	0V	5V	0.475062	0
5V	5V	0V	0.90098	0
5V	5V	5V	0.322235	0

Task02

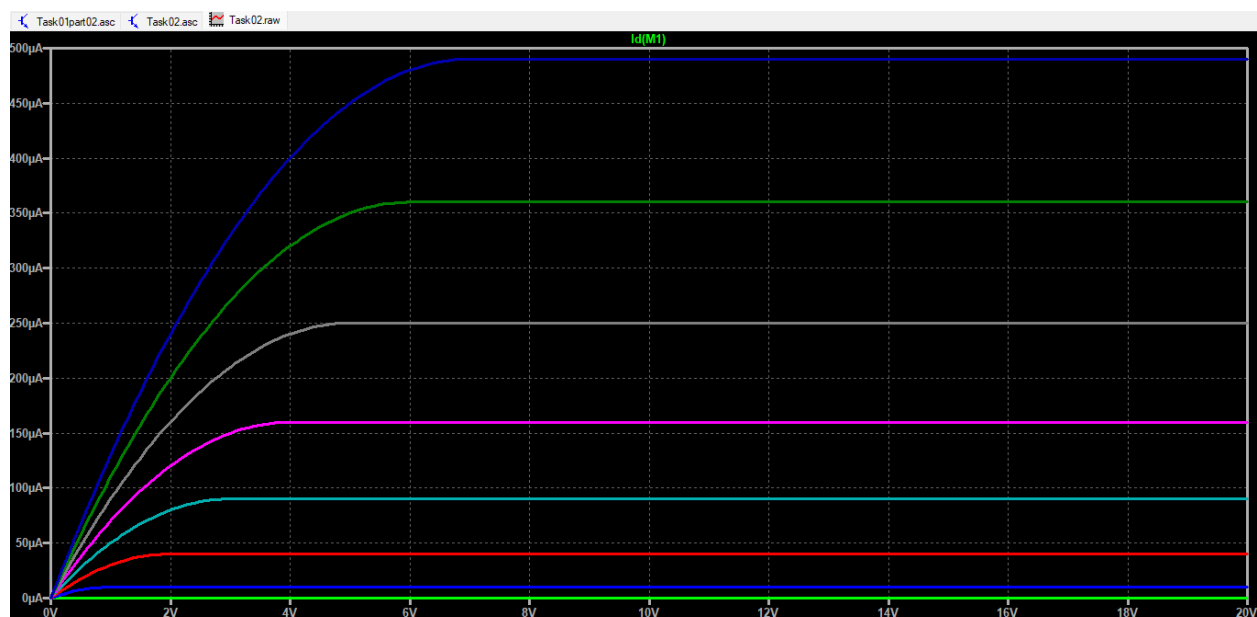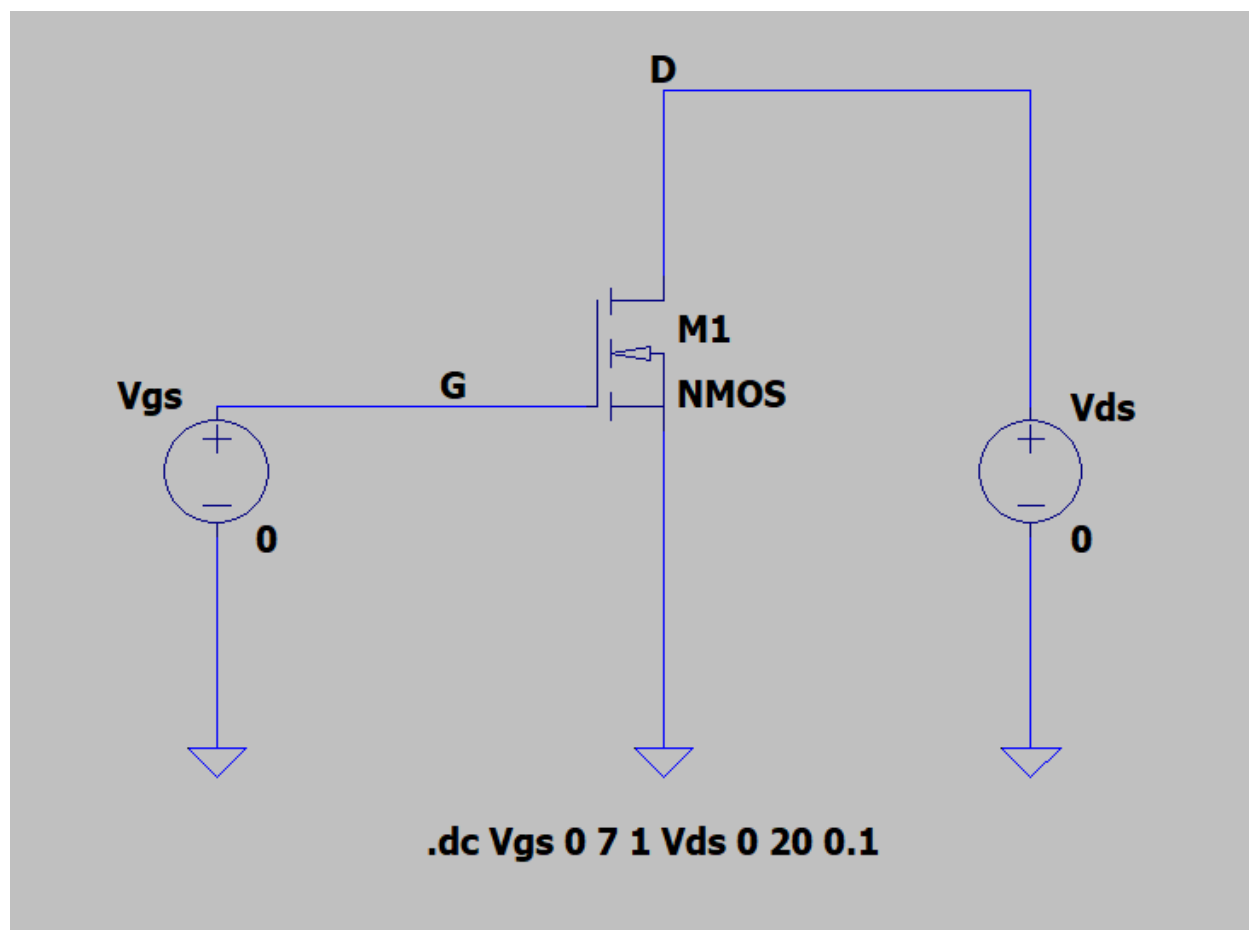

Task03

