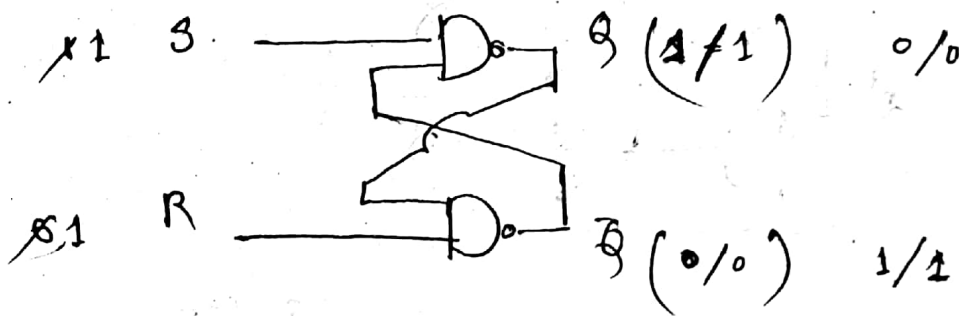


Sequential Circuits

03/28/23

NAND min 1 zero output 1


0	0	1
0	1	1
1	0	1
1	1	0



SR Latch using NAND

S	R	Q	Q'
0	0	Impossible	
0	1	1	0
1	0	0	1
1	1	0	1 [Memory / No change]

S-R Flip flop

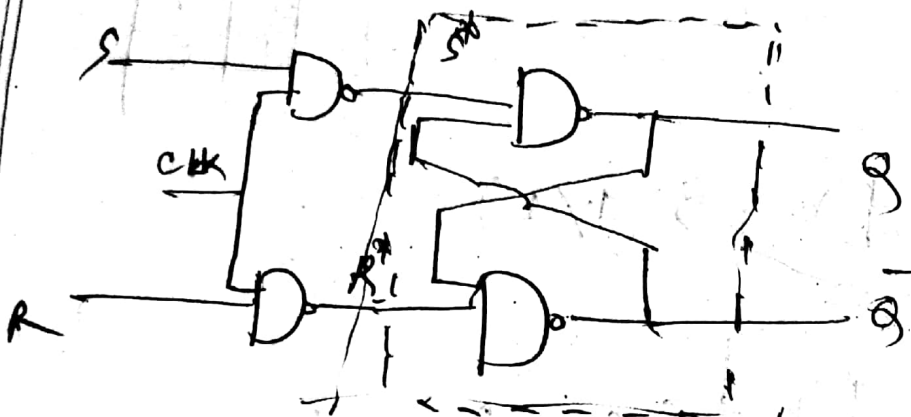

if $\boxed{CLK = 1}$

S = Set
R = Reset

$$S^* = (S \cdot CLK)' = S' + CLK'$$

$$R^* = (R \cdot CLK)' = R' + CLK'$$

$$S^* = S' + 1' = S' + 0 = S'$$

$$R^* = R' + 1' = R' + 0 = R'$$

we get,

$$S^* = S'$$

$$R^* = R'$$

NAND


A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

used in latch

SR F.F

S	R	S*	R*	Q	Q'
0	0	1	1	Memory/ No change	
0	1	1	0	0	1
1	0	0	1	1	0
1	1	0	0	Not used	

S	R	Q	Q'
0	0	Memory/ No change	
0	1	0	1
1	0	1	0
1	1	Not used	

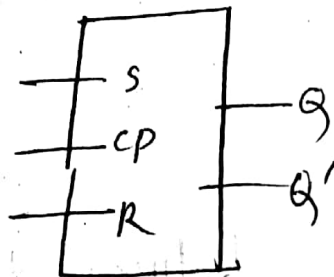

Block Diagram

Characteristics Table

Q(t)	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Next Step

Memory / No change
(Next step = Present)

- 1) Check S R from SR.FF Truth table
2. Q(t+1) acc. Q(t)
- ↳ is from FF.

⊛ Excitation table

P	Q	Q^+	S	R
0	0	0	0	x
0	1	1	1	0
1	0	0	0	1
1	1	1	x	0

D flip flop

D	Q	Q'
0	0	1
1	1	0

from flip flop table
excluding 1st & last row

D flip flop Charac



$Q(t)$	D	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

⊛ Excitation

Q	Q^+	D
0	0	0
0	1	1
1	0	0
1	1	1

J-k flip flop

* Jack ki lip flop

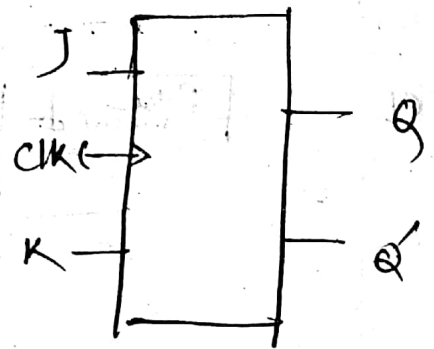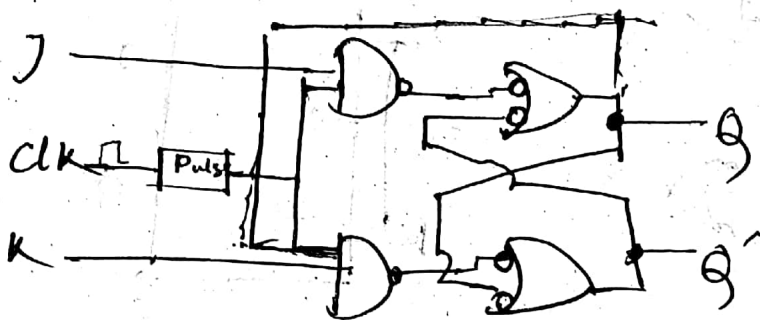

Truth table



J	K	Q	Q'
0	0	Memory / No Change	
0	1	0	1
1	0	1	0
1	1	Toggle	Toggle

Characteristic

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Q	Q'	J	K
0	0	0	X
0	1	1	1
1	0	X	1
1	1	X	0

T-flip flop

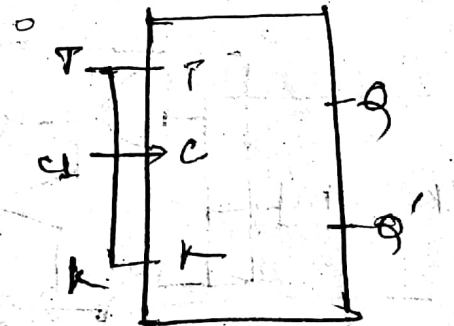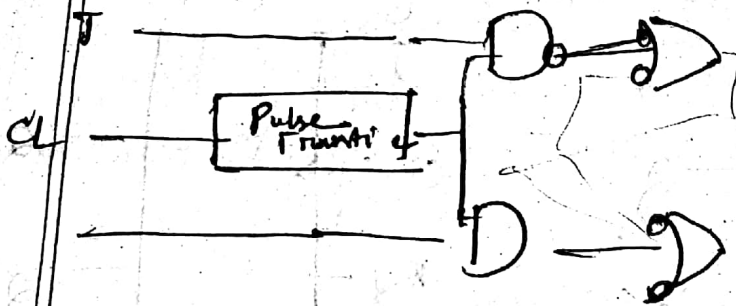

excitation

P.S N.S		FF, TT
Q	Q'	T
0	0	0
0	1	1
1	0	1
1	1	0

truth table

Φ	Q	Q'
0	No Change	
1	Toggle	

Characteristic

Sequential Circuit Analysis

Circuit Diagram to State Diagram :

① Present State : Next Step
 $A \text{ \& } B$ $A^+ \text{ \& } B^+$

Input : Output :
 DA, DB, x y

② Equations :
 $DA = Ax + Bx$
 $DB = A'x$
 $y = (A+B)x'$


③ state table

A	B	x	DA	DB	y	A ⁺	B ⁺
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	0	0	1	0	0
0	1	1	1	1	0	1	1
1	0	0	0	0	1	0	0
1	0	1	1	0	0	1	0
1	1	0	0	0	1	0	0
1	1	1	1	0	0	1	0

t.t for Df.f
 Next Step

0	0
0	0
1	1

④ diagram:

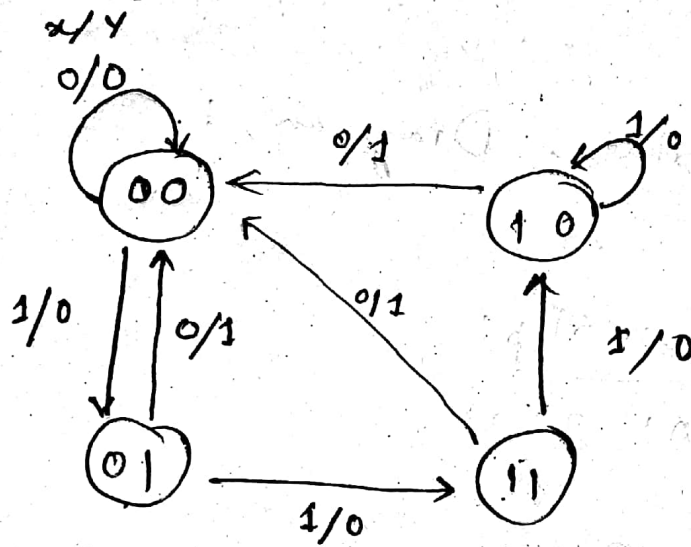

⑤ Using JK

① Present States

A B

Next States

A + B +

Input:

J_A, K_A, J_B, K_B, x

② Equations:

$$J_A = B$$

$$K_A = B'$$

$$J_B = x'$$


$$K_B = A \oplus x$$

③ State table

Inputs			Present States				Next States	
A	B	x	J A	K A	J B	K B	A+	B+
0	0	0					0	1
0	0	1					0	0
0	1	0					1	1
0	1	1					1	0
1	0	0					1	1
1	0	1					1	0
1	1	0					0	0
1	1	1					1	1

T.T. of JK flipflop.

④

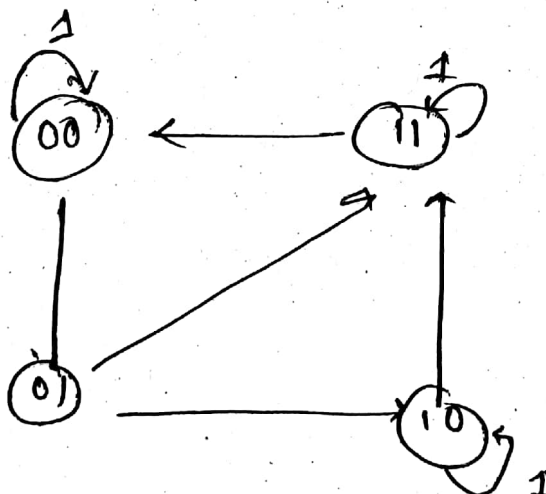

State Diagram to Circuit Diagram



[illegible]

knaps

input J-f function:

$$JA = B \cdot x'$$

$$JB = x$$


$$KA = B \cdot x$$

$$KB = (A \oplus x)'$$

Logic Diagram:

Counters:

① Synchronous (2 bit) ②

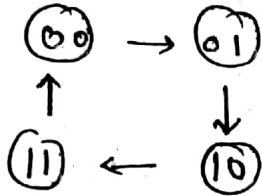

P.S		N.S		F.F. input	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

③

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0



excitation t. of T.f.f.

④

$$TA_1 = 0$$

$$TA_0 = 1$$


present state would be keep input

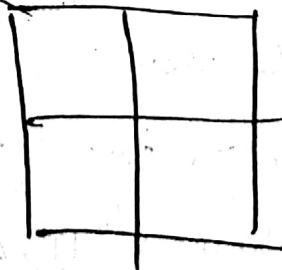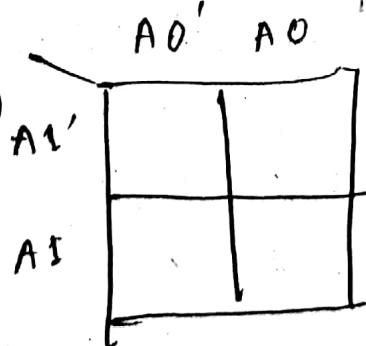

$$TA_1 = A_1' A_0 + A_1 A_0$$

$$A_0$$

$$TA_0 = 1$$

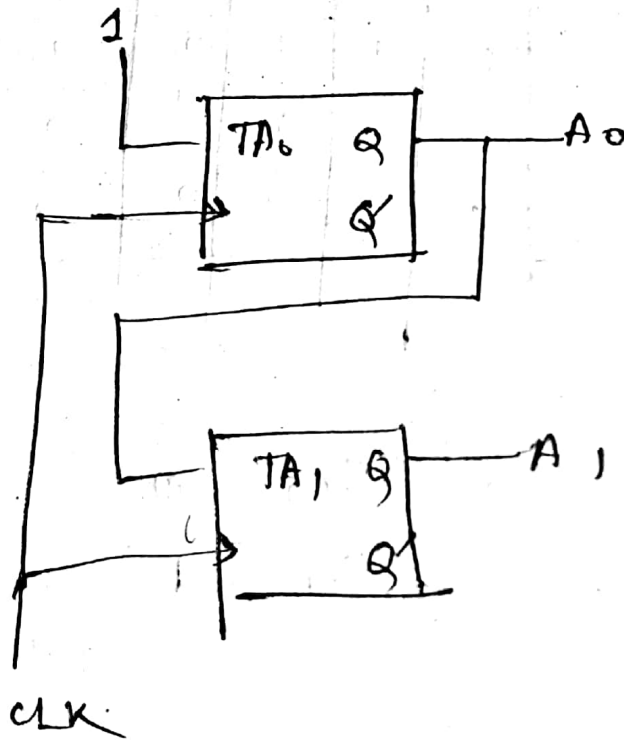

- ① JK sorted = T flipflop
- ② Up Counter
- ③ Down Counter (3 bit)
- ④ Synchronous Up/Down

Slide 30

3 bit synchronous Up/Down Counter




Handwritten notes and equations related to the counter, including the formula for the output of the counter:

$$Y = A \oplus B \oplus C$$

Implementation counter T.F.F.

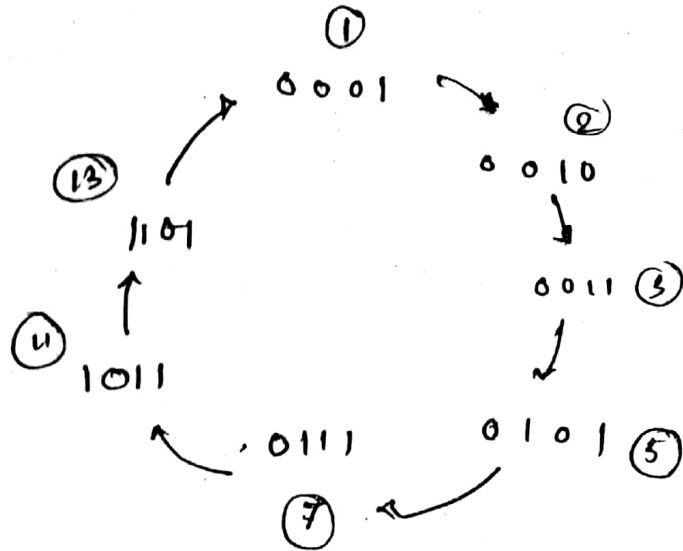$1 \rightarrow 2 \rightarrow 3 \rightarrow 5 \rightarrow 7 \rightarrow 11 \rightarrow 13 \rightarrow 17$



excitation

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

state table

[illegible]

(Imp)

prac slide

Draw Circuits for Kmap functions :

00 $\boxed{01 \rightarrow 010}$ $\boxed{01 \rightarrow 00}$
 Green \rightarrow Yellow \rightarrow Red \rightarrow Yellow \rightarrow Green

00 \rightarrow 01
 01 \rightarrow 10/00
 10 \rightarrow 01

excitation D f.f

q_n	A_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

Present Status			Next State		FF D	
A	B	x	A+	B+	DA	DB
0	0	0	0	1	0	1
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	1	0	1	0	1
1	1	0	x	x	x	x
1	1	1	x	x	x	x

A	Bx	01	11	10
0	0	1	1	1
1	0	x	x	x

A	Bx	01	11	10
0	0	1	1	1
1	0	x	x	x

1 state \rightarrow 3 to state

external input 2 Σ x, y

$2^4 = 16$ possible combination.